

تم ارفعه
بواسطة
م. من
الحوي عيسى

فريداد (2)
اصي ن عاصي

بسم الله الرحمن الرحيم



وزارة التربية والتعليم العالي

Ministry of Education & Higher Education

السلطة الوطنية الفلسطينية

Palestine national Authority

Palestine Technical University-Kadoorie		الاسم: <u>م. من سلام محمود فهدان</u>	
Faculty of Applied Sciences		الرقم الجامعي: <u>22</u>	
General Phys. II, Second Exam(Spring2010)		مدرس المادة: <u>د. صافي جبر</u>	
Date: 17/05/2010	Time: 1 hour	التخصص: <u>الفيزياء</u>	الشعبة: <u>22</u>

Note: $1\mu = 10^{-6}$, $1n = 10^{-9}$ (B)

Q1. Read the following carefully and circle the symbol of the most appropriate answer for each question. (1.5pt. for each of a 10 right answers)

1. Capacitance measures the ability of the capacitor to store:

- a) Charge on its surfaces; b) Electric energy between its surfaces;
c) Electric field between its surfaces; d) All of the above.

2. An air-filled parallel-plate capacitor is fully charged by connecting it to a battery. When the capacitor is disconnected from the battery and a dielectric is inserted between its plates. Which quantity (quantities) remains (remain) the same?

- a) Its potential V; b) Its charge Q; c) Its capacitance C; d) All of them.

3. Three capacitors are connected as shown in Fig. (1), where $C_1 = 2.0 \mu F$, $C_2 = 1.0 \mu F$, $C_3 = 3\mu F$. The equivalent capacitance (in μF) between points a and b is

- a) 2; b) 0.75;
c) 1.5; d) 8.

$$\frac{1}{\frac{1}{2} + \frac{1}{3}} = \frac{2}{\frac{5}{6}} = \frac{12}{5} = 2.4$$

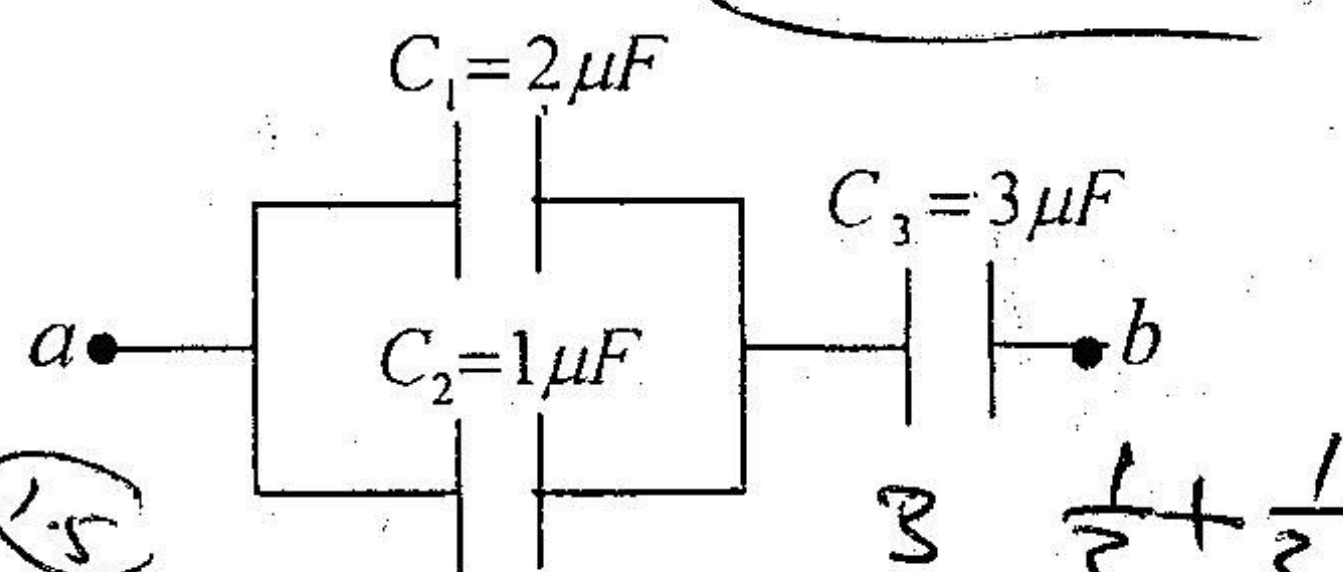


Fig.1

4. A 4.0Ω resistor has potential drop of 8 V across its ends. The quantity of charge (in C) that pass through the resistor in 1 minute is

- a) 180; b) 3;
c) 120; d) 30.

$$R = 4 \Omega, V = 8 \text{ V}, Q = CV, I = \frac{V}{R} = \frac{8}{4} = 2 \text{ A}, Q = I \cdot t = 2 \cdot 60 = 120 \text{ C}$$

5. Electrical conductivity σ of a material depends on:

- a) the applied electric field; b) the geometry of the material;
c) the current density in the material; d) physical quantities of the material;

$$I = nqA v_d$$

$$v_d = \frac{I}{nqA} = \frac{qE\tau}{m}$$

$$\sigma = \frac{nq^2\tau}{m}$$

6. The drift speed v_d in a material depends on:

- a) the current in the material; b) physical quantities of the material;
c) the applied electric field; d) both b and c;

7. When charging a capacitor (Fig.2), the maximum current occurs

- a) at the time equal its time constant;
b) at the moment the circuit is closed;
c) after a long time;
d) the current is constant, so no maximum occurs.

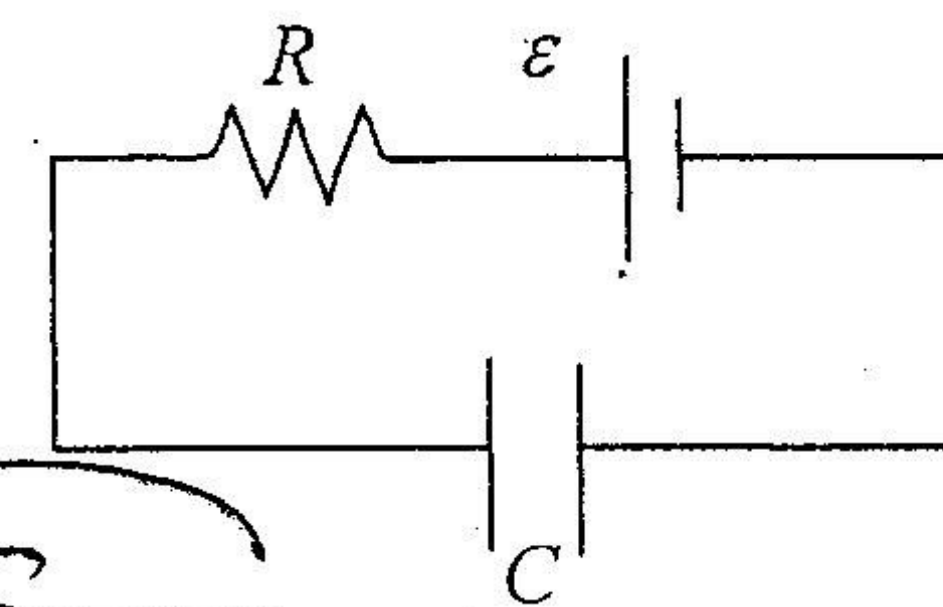


Fig.2

$$I(t) = \frac{\epsilon}{R} e^{-t/RC}$$

$$\text{Energy in } P_s = 2 \times [\text{energy in Capacitor}]$$

8. In Q7 (directly above) the total energy delivered by the power supply in Fig. 2 is

- a) $\frac{1}{2} C \epsilon^2$; b) $2 C \epsilon^2$; c) $C \epsilon^2$; d) $\frac{1}{2} \epsilon C^2$.

9. The time constant in an RC circuit is the time at which

- a) the energy stored becomes $1/e$ of its final value;
 b) the current decreases to $1/e$ of its initial value;
 c) a and b;
 d) the charge becomes $1/e$ of its final value.

$$\tau = RC$$

$$q(t) = 0$$

$$i(t) = 0.368 \left(\frac{\epsilon}{R} \right)$$

$$q(t) = 0.632 C \epsilon$$

10. Kirchhoff's first rule for currents at a junction is a statement of

- a) conservation of energy;
 b) conservation of mass;
 c) conservation of momentum;
 d) conservation charge.

11. In Fig. (3), suppose that the switch has been closed for a long time sufficiently long for the capacitor to become fully charged, the charge Q on the capacitor (in μC) is.

- a) 28; b) 12; c) 4×10^{-6} ; d) 16;

$$q(t) = C \epsilon = 4 \times 10^{-6} \quad \epsilon = I R = \frac{V}{R}$$

Q2. In Fig. 4, the current through the resistor R_2 is $I = 2A$,

- a) What is the value of the currents I_1 and I_2 ? (5pts)
 b) What is the value of ϵ_2 ? (3 pts)
 c) What is the power dissipated in the 3Ω Resistor? (2 pts)

Loop (1) - apply Kirchhoff's Laws

$$10 - 4I_1 - 3(2) = 0$$

$$10 - 6 - 4I_1 = 0$$

$$4 - 4I_1 = 0 \Rightarrow 4 = 4I_1 \Rightarrow$$

$$I_1 = \frac{4}{4} = 1A$$

$$I_1 + I_2 = 2$$

$$1 + I_2 = 2 \Rightarrow I_2 = 1A$$

Loop (2) :-

$$3(2) - \epsilon_2 + 6(1) = 0$$

$$6 - \epsilon_2 + 6 = 0$$

$$\epsilon_2 = 12V$$

c) Power dissipated in the (3Ω) Resistor = $I^2 R = (2)^2 (3) = (4)(3) = 12 \text{ Watt}$

$$I_1 = 1A$$

$$I_2 = 1A$$

$$\epsilon_2 = 12V$$

$$P_{(3\Omega)} = 12 \text{ Watt}$$

End of the questions- Good Luck